



Homework 6

Homework must be done on paper and submitted to the corresponding submitting portal on iLearn! What to submit:

- The schematic of the single cycle CPU with your implementation. Overdrawing of the schematic page of this PDF is totally ok
- A textfile where you explain what's going on.

Exercise:

Take the schematic from the single cycle CPU and add a new instruction "MAX".

It should do following:

MAX \$d, \$s, \$t

$d = \max(s, t);$

So \$d gets either the value of register \$s or \$t depending on which is bigger.

Implement new logic to the schematic to achieve that.

You can implement new lines, muxer and logic gates.

Hints:

- To decide which number is bigger, subtract them with the ALU and decide if the result is bigger than zero (first bit of the 32 bit ALU output is 0 or 1?).
- Set the register chips correct to read/write.
- The op-code has 6 digits. Choose a new one wisely.

